



USN

--	--	--	--	--	--	--	--	--	--

18MT35

Third Semester B.E. Degree Examination, June/July 2024 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat circuit diagram and waveform, explain Double ended shunt clippers. (07 Marks)
- b. Explain the working of positive clampers with neat circuit diagram and waveforms. (05 Marks)
- c. Explain with a neat diagram the working of RC coupled BJT amplifier and also sketch the frequency response curve. (08 Marks)

OR

- 2 a. Explain first order low pass Butterworth filter and derive the gain and phase angle equations. (08 Marks)
- b. Design a low pass filter at a cutoff frequency of 1KHz with a passband gain of 2. Using frequency scaling technique converts 1KHz cutoff frequency of LPF to cutoff frequency of 1.6KHz. Assume C = 0.01µfarad. (06 Marks)
- c. With neat diagram and waveform, explain working of Narrow band reject filter. (06 Marks)

Module-2

- 3 a. What is an Oscillator? Explain basic principle of an oscillator. (06 Marks)
- b. Draw Schmitt Trigger circuit using OP-Amp and explain its operation. (08 Marks)
- c. Explain phase shift oscillator with a neat circuit diagram. (06 Marks)

OR

- 4 a. What is Frequency stability? Explain its significance. (06 Marks)
- b. Draw a neat circuit diagram of Wein bridge oscillator and explain its working. (08 Marks)
- c. Explain Non inverting comparator with a neat circuit diagram and waveform. (06 Marks)

Module-3

- 5 a. In detail explain pin diagram and internal architecture of 555 timer. (10 Marks)
- b. Explain the operation of 555 timer as monostable multivibrator with help of circuit diagram and waveform. (10 Marks)

OR

- 6 a. Explain the operation of 555 timer as Astable multivibrator with the help of circuit diagram and waveform. (10 Marks)
- b. With neat diagram explain any two applications of astable multivibrator. (10 Marks)

Module-4

- 7 a. Using K-map solve
 - i) $V = f(w, x, y, z) = \Sigma(1, 5, 7, 8, 9, 10, 11, 13, 15)$
 - ii) $T = f(w, x, y, z) = \pi(1, 3, 8, 10, 12, 13, 14, 15)$.
- b. Design a full Adder from two half adder. (06 Marks)
- c. Using 8:1 MUX realize $f(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 8 a. What is Multiplexer? Explain with logic diagram quadruple 2 to 1 line multiplexer. (10 Marks)
b. Design BCD to decimal decoder circuit. (10 Marks)

Module-5

- 9 a. Draw SR latch circuit using NOR gates and explain its functioning using truth table. (06 Marks)
b. Explain BCD ripple counter with the help of logic diagram and timing diagram. (08 Marks)
c. Explain T Flip Flop with the help of logic diagram and obtain its characteristic equation. (06 Marks)

OR

- 10 a. Draw logic diagram of JK Flip Flop and explain its operation. Also obtain its characteristic equation. (06 Marks)
b. Explain 4-bit up-down binary counter. (08 Marks)
c. What is Counter? Distinguish between synchronous and ripple counter. Briefly explain 3 bit ripple counter. (06 Marks)
