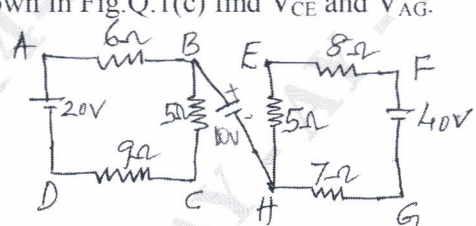
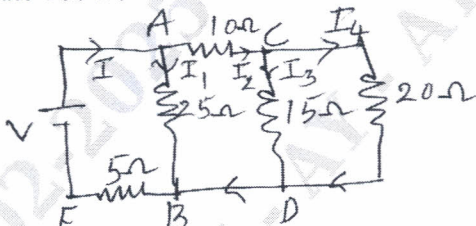


**Second Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025**  
**Introduction to Electrical Engineering**

Time: 3 hrs.

Max. Marks: 100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.*  
*2. VTU Formula Hand Book is permitted.*  
*3. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Explain a typical electric power system with the help of a labeled single line diagram.	8	L2	CO1
	b.	Draw and explain the working of solar photovoltaic power generation system.	6	L2	CO1
	c.	For the circuit shown in Fig.Q.1(c) find $V_{CE}$ and $V_{AG}$ .	6	L3	CO1
 <p align="center">Fig.Q.1(c)</p>					
OR					
Q.2	a.	List the advantages and disadvantages of conventional and non conventional energy sources.	7	L2	CO1
	b.	State and explain Kirchoff's laws as applicable to DC circuits.	5	L2	CO1
	c.	In the circuit of Fig.Q.2(c). Find the value of supply voltage $V$ so that $20\Omega$ resistor can dissipate 180W.	8	L3	CO2
 <p align="center">Fig.Q.2(c)</p>					
Module – 2					
Q.3	a.	Define the following terms applied to quantity AC: i) Average value ii) RMS value iii) Form factor iv) Frequency	6	L1	CO2

	b.	Establish the relation between voltage and current in ac circuit containing RL in series. Draw the vector diagram.	8	L3	CO2
	c.	List the advantages and limitations of 3 $\phi$ AC over 1 $\phi$ AC.	6	L2	CO2
<b>OR</b>					
<b>Q.4</b>	a.	Draw the circuit diagram for three phase star and delta connection. Write the relation between line and phase voltage and currents.	6	L2	CO2
	b.	Define the terms active power, reactive power and apparent power.	6	L1	CO2
	c.	A series circuit with $R = 10\Omega$ , $L = 50 \text{ mH}$ and $C = 100 \mu\text{F}$ is provided with 200 V, 50 Hz supply. Find: i) Impedance ii) Current iii) Power iv) Power factor.	8	L3	CO2
<b>Module – 3</b>					
<b>Q.5</b>	a.	With a neat sketch, explain the principle and operation of a DC generator.	8	L2	CO3
	b.	Derive the EMF equation of DC generator.	6	L3	CO3
	c.	Calculate the emf generated by a 6 pole DC generator having 480 conductors and driven at a speed of 1200 rpm. The flux/pole is 0.012 wb. Assume the generator to be i) Lap wound ii) Wave wound.	6	L3	CO3
<b>OR</b>					
<b>Q.6</b>	a.	Define back emf and explain its significance.	6	L2	CO3
	b.	Derive expression for torque developed in a DC motor.	6	L2	CO3
	c.	Explain speed control of DC motor by i) Armature voltage control method ii) Flux control method.	8	L2	CO3
<b>Module – 4</b>					
<b>Q.7</b>	a.	Derive EMF equation of 1 $\phi$ transformer.	6	L3	CO4
	b.	List the various losses occurring in a transformer, explain how copper loss varies with load.	8	L2	CO4
	c.	500 KVA, 1 $\phi$ transformer has $R_1 = 0.4 \Omega$ , $R_2 = 0.001 \Omega$ , $V_1 = 6600 \text{ V}$ , $V_2 = 400 \text{ V}$ , Iron loss = 3 kW, full load copper loss = 3.858 kW. Determine: i) Efficiency at full load, 0.8 pf lagging.	6	L3	CO4
<b>OR</b>					
<b>Q.8</b>	a.	With a neat sketch, explain how rotating magnetic field is produced in a 3 $\phi$ induction motor.	8	L2	CO4
	b.	With a neat sketch, explain squirrel cage and wound rotor of a 3 $\phi$ induction motor.	6	L2	CO4



	c.	Define slip explain its significance.	6	L2	CO4
<b>Module – 5</b>					
<b>Q.9</b>	a.	With neat circuit and switching table explain the 2 way and 3 way control of lamp.	8	L2	CO5
	b.	With a neat diagram, explain the working of fuse.	6	L2	CO5
	c.	What is earthing? With a neat diagram explain the pipe earthing.	6	L2	CO5
<b>OR</b>					
<b>Q.10</b>	a.	Define tariff, explain 2 part tariff with its advantages and disadvantages.	8	L2	CO5
	b.	What is electric shock? Give the preventive measures against the shock.	6	L2	CO5
	c.	List the power rating of house hold appliances including air conditioners PC's, Laptops, printers, LED bulbs etc. Find the total load installed in a house.	6	L2	CO5

\*\*\*\*\*