



## Fourth Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025 Electrical Drives and Control

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Explain the components of electric drive system with a neat block diagram. Mention its advantages. (10 Marks)
- b. Summarize the working of group drive and individual drive with relevant functional diagram. (10 Marks)

**OR**

- 2 a. Derive an expression for thermal model of an electric motor and plot the heating and cooling curves to represent the same. (10 Marks)
- b. With a neat graph, illustrate the various classes of duty and represent the variation in temperature and torque. (10 Marks)

### Module-2

- 3 a. Demonstrate the relationship between torque and the speed in an electric motor and show the graph with relevant expression. (06 Marks)
- b. Compare the highlights of electric braking with mechanical braking. (06 Marks)
- c. A 220 V DC shunt motor has an armature resistance of  $0.062 \Omega$  and with full field has an end of 215 V at speed of 960 rpm. The motor is driving a load with a torque of 172 Nm. Calculate the minimum speed at which the motor can hold the load by mean by regenerative braking. (08 Marks)

**OR**

- 4 a. Outline the working principle of plugging type of braking process in DC shunt and series motor with a neat circuit. (10 Marks)
- b. Distinguish between the regenerative braking and dynamic braking. (05 Marks)
- c. List and explain various components of load torque with suitable expressions. (05 Marks)

### Module-3

- 5 a. With a neat circuit diagram, explain the working of 3-point starter and mention its advantages and limitations. (10 Marks)
- b. Elaborate on the phase controlled rectifier based power control circuit in DC motors. (10 Marks)

**OR**

- 6 a. Demonstrate the operation of slip-ring induction motor and mention its advantages and limitations. (10 Marks)
- b. With a neat circuit diagram, explain the working of 4-point starter in an electric motor. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-4**

- 7 a. Draw the circuit to control the speed of DC shunt motor and explain the steps involved in variation of field resistance. (10 Marks)  
b. Interpret usage of Ward – Leonard method to control the speed of DC shunt motor over forward and reverse rotations. (10 Marks)

**OR**

- 8 a. Explain the working of silicon controlled rectifier (SCR) with I-V characteristics and a circuit to control speed of a DC motor. (10 Marks)  
b. Outline the operating of DC choppers in speed control of DC motor and list its advantages. (10 Marks)

**Module-5**

- 9 a. Summarize the classification of AC regulators used to control the rms value of ac voltage applied to motor. (08 Marks)  
b. Illustrate the working of 3 phase half wave and full wave AC regulator with a neat circuit diagram. (12 Marks)

**OR**

- 10 a. List the most commonly used inverter power circuit for AC motor drives and briefly explain any two invertors. (10 Marks)  
b. Explain the speed control technique used in three phase induction motor. (10 Marks)

\* \* \* \* \*