

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE35

Third Semester B.E. Degree Examination, Dec.2024/Jan.2025 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Deduce the following in the proper canonical form as mentioned :
 - i) $F = AB + \bar{C}D + A\bar{B}C$ into standard SOP form
 - ii) $Z = W_0(W + X + Y)$ into standard SOP form. (10 Marks)
- b. Reduce the following expression using K-map and implement the same using basic gates.
 - i) $f(a, b, c, d) = \sum m(3, 4, 6, 9, 11, 12, 13, 14, 15)$
 - ii) $f(a, b, c, d) = \prod m(0, 2, 4, 5, 6, 7, 9, 11)$. (10 Marks)

OR

- 2 a. Simplify $f(a, b, c, d) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$ using Quine-McClusky method, find prime implicants and essential prime implicants. (12 Marks)
- b. Reduce the following boolean expression using 5 variable K-map
 $f(a, b, c, d, e) = \sum m(0, 2, 4, 5, 6, 7, 13, 15, 16, 18, 20, 21, 22, 23, 29, 31)$. (08 Marks)

Module-2

- 3 a. Design a combinational circuit to find the 9's complement of a single digit BCD number. Realize the equation using logic gates. (10 Marks)
- b. What is comparator? Design a 2-bit magnitude comparator. (10 Marks)

OR

- 4 a. What is priority encoder? Design 4 input D_0, D_1, D_2 and D_3 encoder with there outputs Y_1, Y_0 and valid input. (10 Marks)
- b. Implement $F(A, B, C, D) = \bar{A}B\bar{D} + ACD + \bar{B}CD + \bar{A}CD$ using 8 to 1 multiplexer. (10 Marks)

Module-3

- 5 a. Explain the operation of master slave J-K flip-flop with logic diagram, truth table, symbol and timing diagram. (12 Marks)
- b. Derive the characteristic equation of SR flip-flop, J-K flip-flop, T-flip-flop and D-flip-flop. (08 Marks)

OR

- 6 a. Explain the operation of gated SR flip-flop using NAND logic. (10 Marks)
- b. Construct T-flip-flop using :
 - i) J-K flip-flop
 - ii) SR flip-flop. (10 Marks)

Module-4

- 7 a. Mention the four different modes of shift register. With a neat block diagram, explain parallel in serial out shift register. (10 Marks)
- b. Design asynchronous 3-bit up/down counter using J-K flip-flop. (10 Marks)

OR

- 8 a. Design synchronous Mod-6 counter using D flip-flop. (10 Marks)
- b. Explain 4-bit universal shift register using 4 to 1 multiplexer with the help of logic diagram. Write a mode control table. (10 Marks)

Module-5

- 9 a. Distinguish between mealy and Moore model with block diagram. Define state variable and excitation variable. (10 Marks)
- b. Explain flash memory concept in detail. Mention its advantages and drawbacks. (10 Marks)

OR

- 10 a. What is ROM? What are various types of ROM? Explain. (10 Marks)
- b. Design a clocked sequential circuit that operates according to the state diagram shown in Fig.Q10(b), implement the circuit using D- flip-flop. (10 Marks)

 


Fig.Q10(b)
