

CBCS SCHEME

BEC304

USN



Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025 Network Analysis

Time: 3 hrs.



Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks , L : Bloom's level , C : Course outcomes.*



Module - 1				M	L	C
Q.1	a.	Three impedances are connected in Delta. Obtain the star equivalent of the network.	7	L3	CO1	
	b.	For the circuit shown in Fig. Q1(b). Find the voltage 'V' at node by using nodal analysis. Fig. Q1(b) <div style="text-align: center;"> </div>	6	L3	CO1	
	c.	Determine the current in 12Ω resistor shown in Fig. Q1(c) using source transformation method. Fig. Q1(c) <div style="text-align: center;"> </div>	7	L3	CO1	
OR						
Q.2	a.	Find the loop currents I_1 , I_2 , and I_3 in the circuit shown in Fig. Q2(a). Fig. Q2(a) <div style="text-align: center;"> </div>	7	L3	CO1	

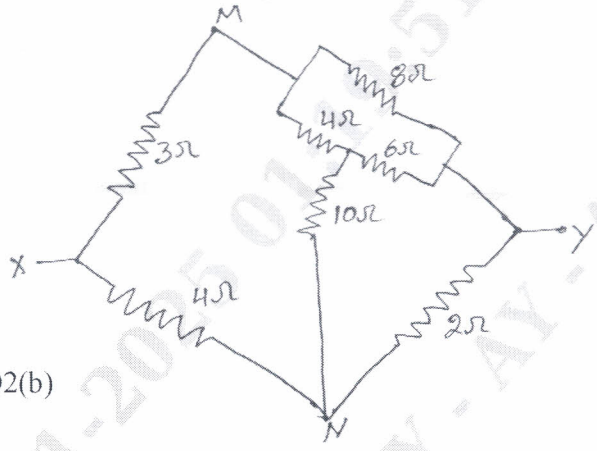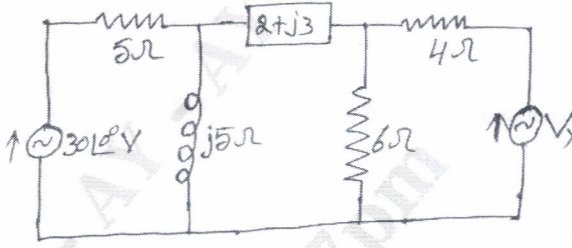	<p>b. Determine the resistance between the terminals X, Y using star delta transformation in the network shown in Fig. Q2(b).</p>  <p>Fig. Q2(b)</p>	6	L3	CO1
	<p>c. Use the nodal analysis to find the value of V_X and the circuit shown in Fig. Q2(c). Such that the current through $(2 + j3) \Omega$ Impedance is zero.</p>  <p>Fig. Q2(c)</p>	7	L3	CO1



Module – 2

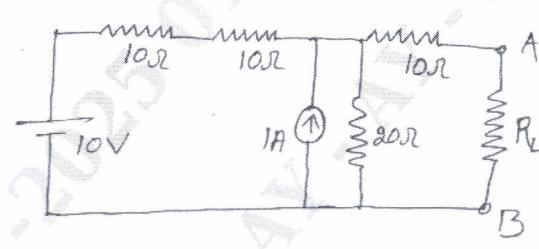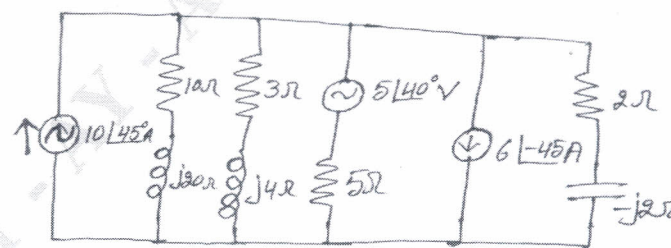Q.3	<p>a. State and prove Superposition theorem.</p>	7	L2	CO2
	<p>b. For the circuit shown in Fig. Q3(b), obtain the Thevenin's equivalent circuit.</p>  <p>Fig. Q3(b)</p>	7	L3	CO2
	<p>c. Using Millman's theorem, find current flowing through $(3 + j4) \Omega$ impedance for the circuit shown in Fig. Q3(c).</p>  <p>Fig. Q3(c)</p>	6	L3	CO2



OR

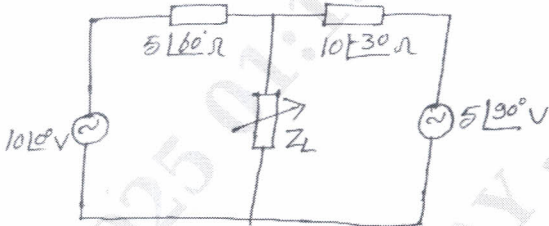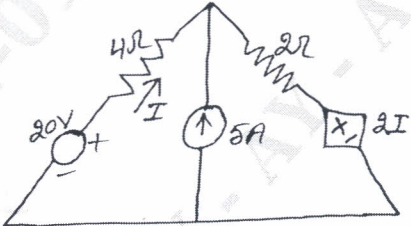Q.4	a. State and prove Norton's theorem.	7	L2	CO2
	<p>b. Find the value of Z_L for Maximum Power transfer and the value of Maximum power for the circuit shown in Fig. Q4(b).</p>  <p>Fig. Q4(b)</p>	6	L3	CO2
	<p>c. Find current 'I' using Super position theorem for the circuit shown in Fig. Q4(c).</p>  <p>Fig. Q4(c)</p>	7	L3	CO2


Module - 3

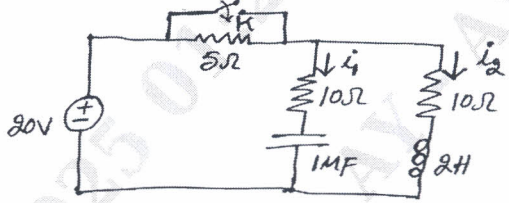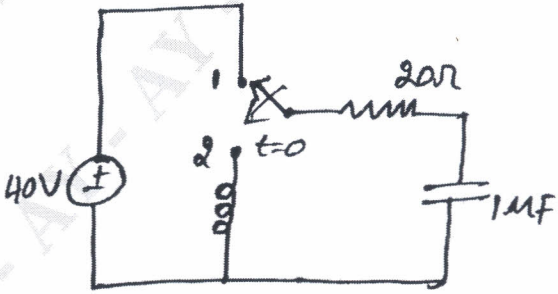Q.5	a. Use the concepts of initial condition to illustrate the voltage behavior in inductor circuit for DC supply.	6	L3	CO3
	<p>b. In the circuit steady state is reached with switch 'K' open. The switch is closed at $t = 0$. Compute i, di/dt and d^2i/dt^2 at $t = 0^+$.</p>  <p>Fig. Q5(b)</p>	7	L3	CO3
	<p>c. The switch is moved from position (1) to position (2) at $t = 0$. The steady state has been reached before switching. Computer i, di/dt and d^2i/dt^2 at $t = 0^+$ for Fig. Q5(c).</p>  <p>Fig. Q5(c)</p>	7	L4	CO3


OR

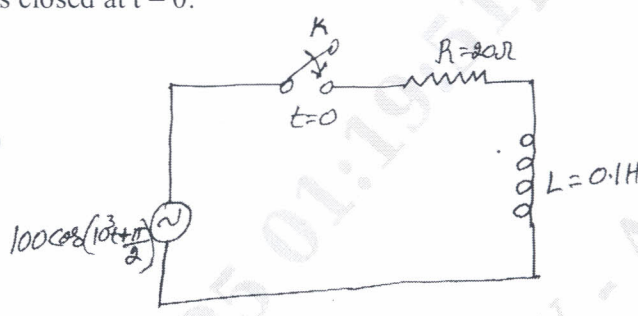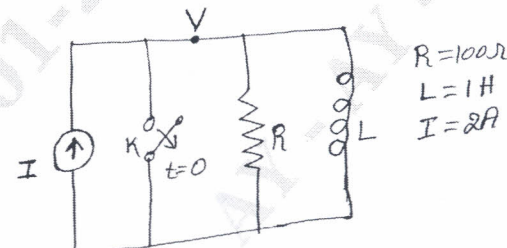
<p>Q.6</p>	<p>a. In the circuit shown in Fig. Q6(a), determine complete solution for current when switch 'K' is closed at $t = 0$.</p>	<p>10</p>	<p>L3</p>	<p>CO3</p>
<p>Fig. Q6(a)</p> 				
	<p>b. Compute v, dv/dt, d^2v/dt^2 at $t = 0^+$ for the circuit shown in below Fig. Q6(b), when the switch K is opened at $t = 0$.</p>	<p>10</p>	<p>L4</p>	<p>CO3</p>
<p>Fig. Q6(b)</p> 				

Module - 4

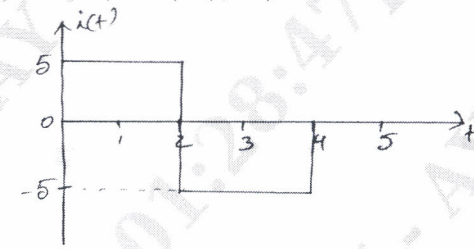
<p>Q.7</p>	<p>a. Using waveform synthesis method to express the voltage pulse in terms of unit step. Find i) $L\{i(t)\}$ ii) $L\{\int i(t).dt\}$.</p>	<p>8</p>	<p>L3</p>	<p>CO4</p>
<p>Fig. Q7(a)</p> 				
	<p>b. State and prove initial value and final value theorem for Laplace transform.</p>	<p>6</p>	<p>L2</p>	<p>CO4</p>
	<p>c. Obtain the Laplace transform of step and ramp function with relevant expressions.</p>	<p>6</p>	<p>L3</p>	<p>CO4</p>

OR


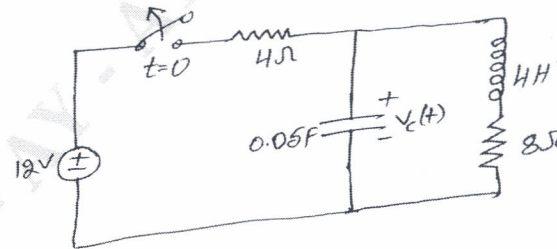
<p>Q.8</p>	<p>a. Determine $i_L(t)$ for $t \geq 0$ using Laplace transform for circuit shown in Fig. Q8(a).</p>	<p>10</p>	<p>L3</p>	<p>CO4</p>
<p>Fig. Q8(a)</p> 				

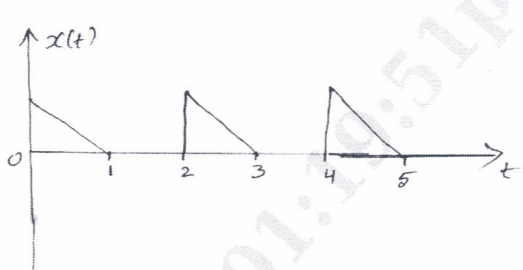	<p>b. Find the Laplace transform of the periodic signal $x(t)$ as shown in Fig. Q8(b).</p>  <p>Fig. Q8(b)</p>	10	L3	CO4
--	--	----	----	-----

Module - 5

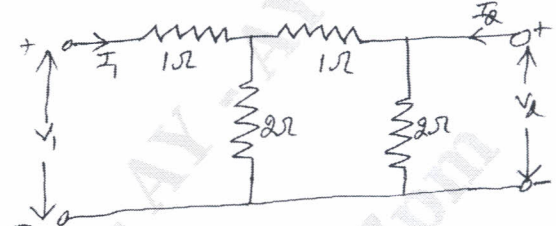Q.9	<p>a. Define Z – parameters. Determine Y parameters interms if Z – parameters.</p>	6	L3	CO5
	<p>b. Show that resonant frequency is geometric mean of cut off frequency in series R – L – C circuit.</p>	7	L3	CO5
	<p>c. Apply the two – port network analysis technique to determine ABCD – parameters of the network shown in Fig. Q9(c).</p>  <p>Fig. Q9(c)</p>	7	L3	CO5

OR

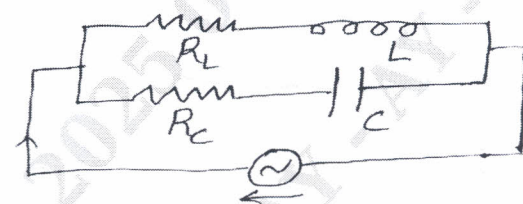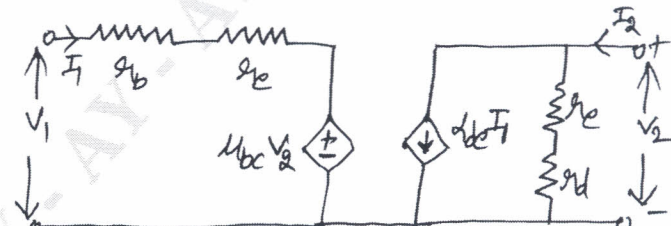Q.10	<p>a. Derive the expression for the resonant frequency of the circuit shown in Fig. Q10(a). Also show that the circuit resonate at all frequency if $R_L = R_C = \sqrt{\frac{L}{C}}$.</p>  <p>Fig. Q10(a)</p>	10	L3	CO5
	<p>b. The model of a transistor in the CE mode is shown in Fig. Q10(b). Determine the h – parameters.</p>  <p>Fig. Q10(b)</p>	10	L3	CO5
