

## Fourth Semester B.E. Degree Examination, Dec.2024/Jan.2025

## Analog Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Derive the expression for Emitter current of a voltage divider bias and also discuss how to make  $I_E$  insensitive to variation in  $\beta$  and temperature. (10 Marks)
- b. Design a collector to Base feedback resistor bias to obtain a dc current of 1 mA and to ensure  $\pm 2V$  signal swing at the collector with  $V_{CE} = 2.3V$ . Assume  $V_{CC} = 10V$  and  $\beta = 100$ . (07 Marks)
- c. What is trans-conductance of BJT and mention its significance? (03 Marks)

## OR

- 2 a. Obtain the following expression of a BJT of small signal analysis.
  - i) Total instantaneous collector current
  - ii) Input resistance at the base
 (10 Marks)
- b. Discuss the following biasing scheme used in MOS
  - i) By fixing  $V_{GS}$
  - ii) By fixing  $V_{GS}$  and connecting a resistance in the source.
 (10 Marks)

Module-2

- 3 a. Discuss the basic configuration of MOSFET. (06 Marks)
- b. For a common source amplifier shown in Fig Q3(b), determine  $R_{in}$ ,  $AV_0$ ,  $R_0$  and  $G_V$

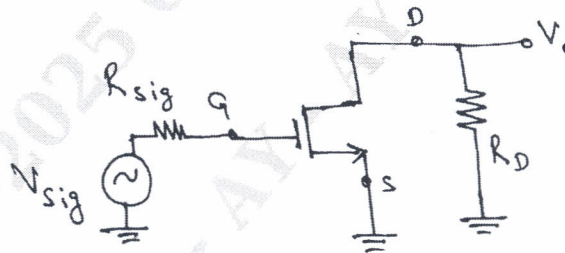


Fig Q3(b)

(14 Marks)

## OR

- 4 a. For an n-channel MOSFET with  $t_{ox} = 10nm$ ,  $L = 1.0 \mu m$ ,  $W = 10 \mu m$ ,  $L_{OV} = 0.05 \mu m$ ,  $C_{sbo} = C_{dbo} = 10 fF$ ,  $V_0 = 0.6V$ ,  $V_{SB} = 1V$  and  $V_{DS} = 2V$ . Calculate  $C_{ox}$ ,  $C_{ov}$ ,  $C_{gs}$ ,  $C_{gd}$ ,  $C_{sb}$  and  $C_{db}$ . (10 Marks)
- b. Explain the working of FET based phase shift oscillator and also mention the necessary conditions for sustained oscillation. (10 Marks)

**Module-3**

- 5 a. Explain the following properties of Negative. Feedback.  
 i) Gain, De-sensitivity ii) Bandwidth Extension iii) Noise reduction (14 Marks)
- b. A negative feedback amplifier has a  $A_f = 100$  and  $A = 10^5$ . What is the feedback factor? If a manufacturing error results in a reduction of  $A$  to  $10^3$ , what is the closed loop voltage Gain? What is the percentage change in  $A_f$ ? (06 Marks)

**OR**

- 6 a. Explain the working of class B output stage. (08 Marks)
- b. For emitter follower Class A output stage  $V_{cc} = 10V$ ,  $I = 100 \text{ mA}$  and  $R_L = 100 \Omega$ . If the output voltage is an 8 V – peak sinusoid, find :  
 i) Power delivered to load  
 ii) Average power drawn from the supplies  
 iii) Power conversion efficiency ignore the loss on  $Q_3$  and  $R$ . (06 Marks)
- c. Explain how cross over distortion can be eliminated to class AB output stage. (06 Marks)

**Module-4**

- 7 a. For the voltage Seri feedback amplifier, derive the expressions of  
 i) Exact voltage Gain ii) Input resistance with feedback iii) Output resistance with feedback (14 Marks)
- b. For the inverting amplifier  $R_1 = 470 \Omega$  and  $R_F = 4.7 \text{ K}\Omega$ . Assume  $A = 200000$ ,  $R_i = 2 \text{ M}\Omega$ ,  $R_o = 75 \Omega$  and  $f_o = 5 \text{ Hz}$ . Calculate  $A_F$ ,  $R_{iF}$ ,  $R_{oF}$  and  $f_F$ . (06 Marks)

**OR**

- 8 a. Explain the working of instrumentation amplifier using Transducer bridge with necessary equations. (08 Marks)
- b. Explain the working of Inverting Schmitt trigger with input and output waveforms. (08 Marks)
- c. For a Differential configuration summer  $R = 1 \text{ K}\Omega$ ,  $V_a = 2V$ ,  $V_b = 3V$ ,  $V_c = 4V$ ,  $V_d = 5V$  and supply voltage of  $\pm 15V$ . Determine the output voltage  $V_o$ . (04 Marks)

**Module-5**

- 9 a. Derive the expression of output voltage of a 4-bit Binary weighted resistor type DAC. Mention its disadvantages. (10 Marks)
- b. Draw the block diagram of successive approximation ADC and explain it. (10 Marks)

**OR**

- 10 a. Explain the working of First order active Lowpass filter with the help of magnitude voltage gain and also design to get a cutoff frequency of 1 KHz with a passband gain of 2. (10 Marks)
- b. Explain the working of Astable multi-vibration using 555 Timer and also derive the expression of Frequency of oscillation. (10 Marks)

\* \* \* \* \*