



## Third Semester B.E. Degree Examination, June/July 2025

### Power Electronics and Instrumentation

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

#### Module-1

- 1 a. Define power electronics and discuss the applications of power electronics. (06 Marks)
- b. Explain the operation of SCR with VI characteristics. (08 Marks)
- c. Discuss various types of turn ON methods for SCR. (06 Marks)

#### OR

- 2 a. Define commutation differentiate natural and forced commutation. (06 Marks)
- b. With neat circuit diagram, explain the operation of full wave RC firing circuit for SCR. (08 Marks)
- c. Discuss basic operation of UJT. (06 Marks)

#### Module-2

- 3 a. With neat circuit diagram, explain the operation of  $1\phi$  half wave phase controlled rectifier with resistive load. (10 Marks)
- b. Explain the followings with respect to choppers : (10 Marks)
  - i) Step up chopper
  - ii) Step down chopper.

#### OR

- 4 a. Classify the choppers based on the operating quadrants and discuss. (10 Marks)
- b. Explain the operation of full wave phase controlled rectifier with resistive load. (10 Marks)

#### Module-3

- 5 a. Explain the operation of  $1\phi$  full bridge inverter with  $R_L$  load. (10 Marks)
- b. Explain the operation of buck converter with circuit diagram. (10 Marks)

#### OR

- 6 a. Discuss the various types of static error in measurements. (10 Marks)
- b. With neat diagram, explain multirange ammeter and voltmeter. (10 Marks)

#### Module-4

- 7 a. With the help diagram, explain the operation of successive approximation type of digital voltmeter. (10 Marks)
- b. Explain dual slope integrating type of DVM. (10 Marks)

#### OR

- 8 a. Describe with block diagram the operation of digital frequency meter. (10 Marks)
- b. Explain the followings: (10 Marks)
  - i) Wheat stone bridge
  - ii) Wein bridge.

**Module-5**

- 9 a. With neat diagram, explain the operation of LVDT. (10 Marks)  
b. Describe the followings:  
i) Electrical transducer parameters  
ii) Resistive position transducer. (10 Marks)

**OR**

- 10 a. With neat structure explain the operation of PLC. (10 Marks)  
b. Explain operation of instrumentation amplifier using transducer bridge. (10 Marks)

\*\*\*\*\*