



Sixth Semester B.E./B.Tech. Degree Examination, June/July 2025
Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Illustrate the peripheral effects of power electronic equipments. (07 Marks)
- b. Using neat diagram, explain diode rectifier circuit. (07 Marks)
- c. Describe static switches. (06 Marks)

OR

- 2 a. Illustrate the relationship of power electronics and control. (06 Marks)
- b. Classify the power electronic circuits and explain DC to AC inverter circuit. (07 Marks)
- c. With neat block diagram, explain typical power electronic convertor. (07 Marks)

Module-2

- 3 a. Using cross section of PNP, and split section at NPN and PNP describe thyristors. (07 Marks)
- b. Explain di/dt and dv/dt protection in thyristors. (07 Marks)
- c. Discuss gate turn off thyristors. (06 Marks)

OR

- 4 a. Using neat diagram, explain V-I characteristic of thyristors. (07 Marks)
- b. Discuss two transistor model of thyristor. (05 Marks)
- c. Compare Natural and forced commutation technique and explain self or load commutation technique. (08 Marks)

Module-3

- 5 a. Write a brief note on AC voltage controller and explain two different types of power transistor control. (06 Marks)
- b. Illustrate the single phase full wave controller with resistive load. (07 Marks)
- c. Describe single phase full converter. (07 Marks)

OR

- 6 a. What are controlled rectifiers and explain with example two different types of phase control converters. (06 Marks)
- b. Write note on semi, full and dual converters. (06 Marks)
- c. Using neat diagram, explain single phase full move controller with R-L-load. (08 Marks)

Module-4

- 7 a. Explain the performance parameters of DC + DC converters. (06 Marks)
- b. Illustrate the step down chopper circuit using resistive load. (07 Marks)
- c. Discuss class-B chopper or second quadrant converter. (07 Marks)

OR

- 8 a. Write a brief note on converter classification along with the diagram. (07 Marks)
- b. Explain step-up chopper circuit. (07 Marks)
- c. Describe different methods at control in the operation of chopper circuit. (06 Marks)

Module-5

- 9 a. Illustrate the principle operation of an inverter. (08 Marks)
- b. Write a note on :
 i) Harmonic Factor n^{th} harmonic (HF_n)
 ii) Total Harmonic Distortion
 iii) Distortion Factor (12 Marks)

OR

- 10 a. Using neat diagram, explain single phase full bridge inverter. (10 Marks)
- b. Write a note on : Single pulse width modulation. (10 Marks)

* * * * *