

USN

--	--	--	--	--	--	--	--	--	--

18ELE13/23

## First/Second Semester B.E. Degree Examination, June/July 2025 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

**Note:** 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. Assume any suitable missing data.

### Module-1

- 1 a. Define the basic laws that are used to study electrical circuits. Give examples. (08 Marks)
- b. With a neat diagram explain the principle of generation of AC voltage. (06 Marks)
- c. Find the current in all the resistors as shown in the figure below.

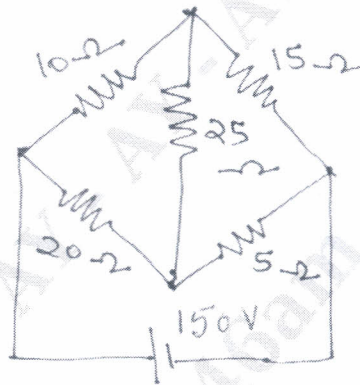


Fig. Q.1(c)

OR

- 2 a. Derive equations for equivalent resistance connected in
  - i) Series
  - ii) Parallel (use 3 resistors  $R_1$ ,  $R_2$ ,  $R_3$ )
- b. With explanation derive the equation for rms value of an AC current. (08 Marks)
- c. An alternating current of frequency 60 HZ has a maximum value of 12A.
  - i) Write the equation for instantaneous value
  - ii) Value of the current at  $\frac{1}{360}$  sec
  - iii) Time taken to reach a value of 9.6A.

### Module-2

- 3 a. Derive the equation for power consumed in a series RC circuit. Draw the relevant phasor diagram and waveforms. (08 Marks)
- b. A voltage of 125 v at 60Hz is applied across a mass inductive resistor connected in series with a capacitor. The current shown is 2.2A. The power loss in the resistor is 96.8 watts and across the capacitor is nil. Calculate the value of resistances and capacitance. (06 Marks)
- c. For a  $\Delta$  connected 3 phase system derive the relation between live and phase current. (06 Marks)

OR

- 4 a. In a pure capacitive circuit, show that power consumed is zero, using relevant equations. (06 Marks)
- b. Show that two wattmeter are sufficient to measure  $3\phi$  power for balanced star connected load. (08 Marks)
- c. Two wattmeter are connected to measure the input of a 15HP, 50Hz  $3\phi$  induction motor at full load. The full load efficiency and power factor are 0.9 and 0.8 lag respectively. Find the reading of the 2 wattmeters. (06 Marks)

Module-3

- 5 a. Classify the transformers depending on  
i) Voltage  
ii) Construction. Draw the required diagram. (08 Marks)
- b. What is earthing? Explain pipe earthing. (06 Marks)
- c. Derive the emf equation of a single phase transformer. (06 Marks)

OR

- 6 a. Explain 3 way control of lamp. (06 Marks)
- b. A single phase transformer has a power factor of 0.8 and an efficiency of 94% at  $\frac{3}{4}$  full load and full load. Full load output is 600 KW. Determine efficiency at  $Y_2$  FL units power factor. (08 Marks)
- c. Write a note on different losses that occurring in a single phase transformer. (06 Marks)

Module-4

- 7 a. Derive the emf equation of DC generator. Write the equation for the terminal voltage, for d.c. shunt generator considering voltage drop. (10 Marks)
- b. Derive the Torque equation of a DC motor. (10 Marks)

OR

- 8 a. With relevant circuit diagram derive the back emf equation for DC series and DC shunt motor. Mention the voltage drops. (10 Marks)
- b. A 4 pole DC shunt generator with lap connected armature has field and armature resistance of  $50\Omega$  and  $0.1\Omega$  respectively. If the generator supplied 60,100v, 40 watt lamps, calculate the total armature current, current in each parallel path and generated emf. Take 1v per brush as BCD. (10 Marks)

Module-5

- 9 a. With neat diagram explain the types of rotor construction of a synchronous generator. List one application of each. (06 Marks)
- b. Explain the concept of rotational magnetic field in an Induction motor. (08 Marks)
- c. A 12 pole  $3\phi$ , alternator is coupled to an engine running at 500 rpm. It supplies an Induction motor which has a full load speed of 1440 rpm. Find  
i) % slip  
ii) No. of poles (06 Marks)

OR

- 10 a. Derive the emf equation of an alternator. (06 Marks)
- b. A 24 pole alternator has a star connected winding with 144 slots and 10 conductors per slot. Its speed is 250 rpm. The winding is full pitched and  $k_d = 0.966$  flux per pole and 67.3 mwb. Determine  
i) The frequency and magnitude of line voltage  
ii) Output KVA of the machine if current in each plate is 50A. (08 Marks)
- c. With neat diagram explain the working of a star Delta starter. (06 Marks)