

First/Second Semester B.E. Degree Examination, June/July 2025 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the working of PN junction diode under forward and reverse bias condition. (06 Marks)
- b. Explain with a neat diagram and waveform, the working of full wave bridge rectifier. (08 Marks)
- c. Explain equivalent circuit of diode with necessary diagram. (06 Marks)

OR

- 2 a. Show that the efficiency of full wave bridge rectifier is 81.2%. (06 Marks)
- b. Explain how zener acts as voltage regulator. (06 Marks)
- c. Explain the working of half wave with and without capacitor filter with necessary waveforms. (08 Marks)

Module-2

- 3 a. Explain drain and transfer characteristics of JFET with necessary diagram. (10 Marks)
- b. Explain the construction and working of enhancement type MOSFET. (10 Marks)

OR

- 4 a. Explain the V-I characteristics of SCR with necessary waveform. (10 Marks)
- b. Explain digital circuit applications of CMOS. (10 Marks)

Module-3

- 5 a. Define the terms :
 - i) Voltage follower
 - ii) Virtual ground
 - iii) CMRR
 - iv) Slewrate
 - v) Input bias current. (10 Marks)
- b. Explain the operation of an OPAMP an inverting amplifiers and write the necessary output waveform V_0 for an input $V_{in} = 1V$ and gain $A_v = 10$. (10 Marks)

OR

- 6 a. Explain how OPAMP can be used as integrator and differentiator with necessary waveform. (10 Marks)
- b. Explain the operation of an adder circuit to meet the equation $V_0 = -[V_1 + V_2 + V_3]$. (10 Marks)

Module-4

- 7 a. Explain the properties and advantages of negative feedback amplifier. (10 Marks)
- b. Explain the working principle of phase shift oscillator with necessary diagram. (10 Marks)

OR

- 8 a. List out the classification of oscillator. (08 Marks)
 b. Explain the operation of IC555 as astable oscillator with necessary diagram, and waveform and also derive its charging and discharging time of the circuit. (12 Marks)

Module-5

- 9 a. Find :
 i) $(1101011101101010)_{16} = (?)_8$
 ii) $(EB986)_{16} = (?)_8$
 iii) $(925.75)_{10} = (?)_2$
 iv) $(745.36)_8 = (?)_{10}$
 v) Subtract (10101) from $(101010) = (?)_{10}$ (10 Marks)
 b. What is flip flop? Explain the operation of master-slave JK flip flop. (10 Marks)

OR

- 10 a. Explain the basic elements of communication system with block diagram. (10 Marks)
 b. Prove that
 i) $\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$
 ii) $\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$ (10 Marks)
